

Measurement of S/Z/Y parameters

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \text{ (o.c. port 2)}, \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \text{ (o.c. port 1)}, \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \text{ (s.c. port 2)}, \quad Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}, \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$S_{11} = \frac{b_1}{a_1} \Big|_{a_2=0} \text{ (Matched port 2)}, \quad S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0}$$

$$S_{12} = \frac{b_1}{a_2} \Big|_{a_1=0}, \quad S_{22} = \frac{b_2}{a_2} \Big|_{a_1=0}$$


Network analyzers providing

- phase and magnitude
 - ↳ vector analyzers
- magnitude only
 - ↳ scalar analyzers

Cascaded Two Ports

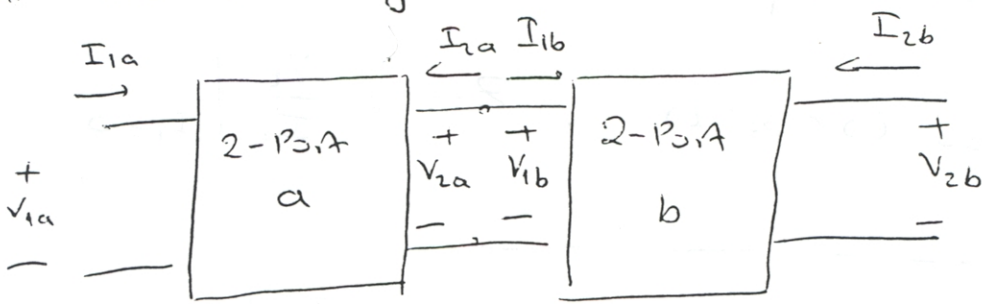(2)

ABCD and T-matrix are especially useful when two ports are connected in tandem or cascade. (Output of one network becomes input of the following network)



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}, \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

and: $V_{2a} = V_{1b}$, $-I_{2a} = I_{1b}$

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

Transfer Matrix of the
two cascaded networks

N-networks in cascade:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \dots \begin{bmatrix} A_N & B_N \\ C_N & D_N \end{bmatrix}$$

Similarly for T matrix starting from the last unit, since they give output in terms of input:

$$\begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} = \begin{bmatrix} (T_{11})_b & (T_{12})_b \\ (T_{21})_b & (T_{22})_b \end{bmatrix} \begin{bmatrix} (T_{11})_a & (T_{12})_a \\ (T_{21})_a & (T_{22})_a \end{bmatrix}$$


(3)

and generalizing:

$$\begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} = \begin{bmatrix} (T_{11})_N & (T_{12})_N \\ (T_{21})_N & (T_{22})_N \end{bmatrix} \dots \begin{bmatrix} (T_{11})_1 & (T_{12})_1 \\ (T_{21})_1 & (T_{22})_1 \end{bmatrix}$$

Examples for ABCD


(A) Transmission Line

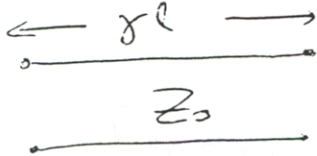

$$\begin{aligned} A &= \cosh \gamma l \\ B &= Z_0 \sinh \gamma l \\ C &= Y_0 \sinh \gamma l \\ D &= \cosh \gamma l \end{aligned}$$


$$\begin{aligned} \sinh x &= \frac{e^x - e^{-x}}{2} \\ \cosh x &= \frac{e^x + e^{-x}}{2} \\ \cosh^2 x - \sinh^2 x &= 1 \end{aligned}$$

(B) Ideal Transformer


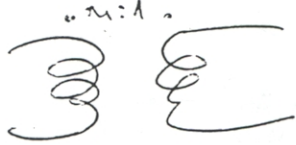


$$\begin{aligned} A &= n \\ B &= 0 \\ C &= 0 \\ D &= 1/n \end{aligned}$$


(C) Series Impedance

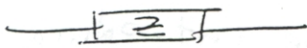
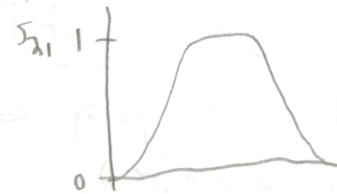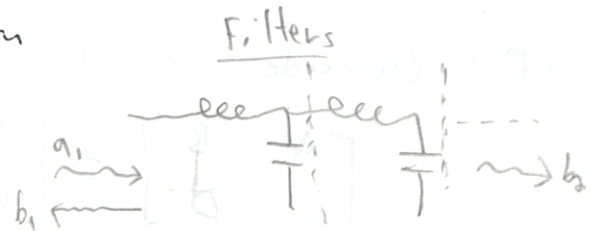
$$\begin{aligned} A &= 1 \\ B &= Z \\ C &= 0 \\ D &= 1 \end{aligned}$$




(D) Shunt Admittance

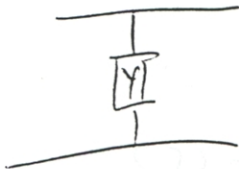

$$\begin{aligned} A &= 1 \\ B &= 0 \\ C &= Y \\ D &= 1 \end{aligned}$$

RF - filters - periodic

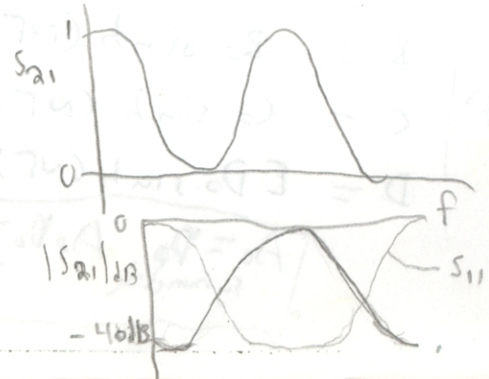


7 really: $|S_{11}|^2 + |S_{21}|^2 = 1 \rightarrow |S_{11}|^2 = 1 - |S_{21}|^2$

$|a|^2 = |b_1|^2 + |b_2|^2$ refl. transh.

$1 = \frac{|b_1|^2}{|a|^2} + \frac{|b_2|^2}{|a|^2} = |S_{11}|^2 + |S_{21}|^2$

→ (E) Transm. Line with Shunt Admittance

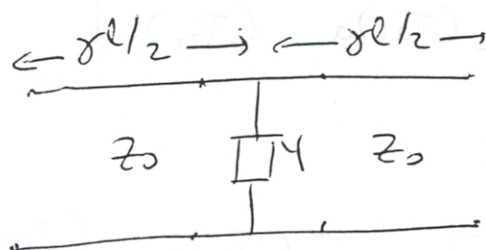

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh\left(\frac{\gamma l}{2}\right) & Z_0 \sinh\left(\frac{\gamma l}{2}\right) \\ Y_0 \sinh\left(\frac{\gamma l}{2}\right) & \cosh\left(\frac{\gamma l}{2}\right) \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} \cosh\left(\frac{\gamma l}{2}\right) & Z_0 \sinh\left(\frac{\gamma l}{2}\right) \\ Y_0 \sinh\left(\frac{\gamma l}{2}\right) & \cosh\left(\frac{\gamma l}{2}\right) \end{bmatrix}$$

$$\left\{ \begin{aligned} \sinh(2x) &= 2 \sinh(x) \cosh(x) \\ \cosh(2x) &= \cosh^2 x + \sinh^2 x = 2 \cosh^2 x - 1 \\ &= 1 + 2 \sinh^2 x \end{aligned} \right.$$

$$A = D = \cosh \gamma l + \left(\frac{Y}{2Y_0}\right) \sinh \gamma l$$


$$B = Z_0 \left[\left(\frac{Y}{2Y_0}\right) (-1 + \cosh \gamma l) + \sinh \gamma l \right]$$

$$C = Y_0 \left[\left(\frac{Y}{2Y_0}\right) (1 + \cosh \gamma l) + \sinh \gamma l \right]$$

Lect. 28

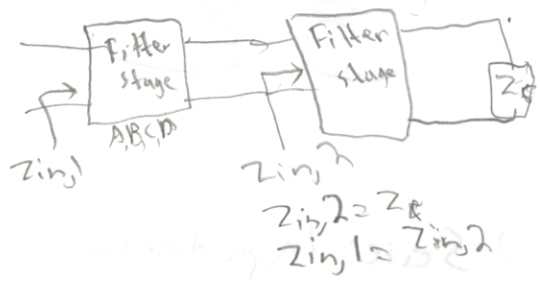(F) Cascade of N Two-Ports

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix}^N$$



Defining: $\cosh \Gamma = (A_0 + D_0) / 2$, we introduce the

"effective prop. constant" of the network (charact. root of the matrix). Algebraically for a reciprocal network:

For cascade of stages

$$\begin{aligned} A &= [A_0 \sinh(N\Gamma) - \sinh((N-1)\Gamma)] / \sinh(\Gamma) \\ B &= B_0 \sinh(N\Gamma) / \sinh(\Gamma) \\ C &= C_0 \sinh(N\Gamma) / \sinh(\Gamma) \\ D &= [D_0 \sinh(N\Gamma) - \sinh((N-1)\Gamma)] / \sinh(\Gamma) \end{aligned}$$

$$A_0 = D_0 \quad A_0 D_0 - B_0 C_0 = 1$$

symmetric reciprocal

TABLE 5.2 Conversions Between Two-Port Network Parameters

	S	Z	Y	ABCD
S_{11}		$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{11}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}		$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}		$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{A + B/Z_0 + CZ_0 + D}{-A + B/Z_0 - CZ_0 + D}$
S_{22}		$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 + CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
Z_{11}	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	$Z_0 \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}$	Z_{22}	$\frac{ Y }{Y_{11}}$	$\frac{D}{C}$
Y_{11}	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC - AD}{B}$
Y_{21}	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) - S_{12}S_{21}}{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	A
B	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	B
C	$\frac{1 - (1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{Z_0}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	C
D	$\frac{(1 - S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{21}}{Z_{22}}$	$\frac{Y_{21}}{-Y_{11}}$	D

$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}$; $|Y| = Y_{11}Y_{22} - Y_{12}Y_{21}$; $\Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}$; $\Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}$; $Y_0 = 1/Z_0$

Assume that each cell is symmetric: $A_0 = D_0$
and reciprocal: $A_0 D_0 - B_0 C_0 = 1$

Terminate the chain in a characteristic impedance Z_c such that each cell terminated in Z_c gives impedance Z_c at its input:

$$Z_c = \frac{V_1}{I_1} = \frac{A_0 V_2 - B_0 I_2}{C_0 V_2 - A_0 I_2} = \frac{A_0 Z_c + B_0}{C_0 Z_c + A_0}$$

$\gamma, \Gamma, Z_0, \gamma = \Gamma, Z_0, \Gamma, \gamma = 1$

replace w/ transmission line

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_0 \sinh(\gamma l) \\ \frac{1}{Z_0} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix}$$

$$Z_c = \left(\frac{B_0}{C_0}\right)^{1/2} \quad (\neq A_0)$$

$$\begin{cases} A = D = \cosh N\Gamma \\ B = Z_c \sinh N\Gamma \\ C = (Z_c)^{-1} \sinh N\Gamma \end{cases}$$

$$\begin{pmatrix} \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix} \\ \cosh \Gamma = (A_0 + D_0)/2 \end{pmatrix}$$

(Each cell acts as a transmission line of char. impedance Z_c and overall prop. constant Γ)

Cascaded N sections have overall prop. constant $N\Gamma$

passband/rejection band determined by single stage

$$|\cosh \Gamma| = |(A_0 + D_0)/2|$$


- $\leq 1 \Rightarrow \Gamma$ imaginary \Rightarrow no attenuation (only time shift)
- $> 1 \Rightarrow \Gamma$ real and there is attenuation

Filter!


Microwave and Optical Filters

Pass desired frequencies with small attenuation
 Much higher attenuation for noise and undesired signal

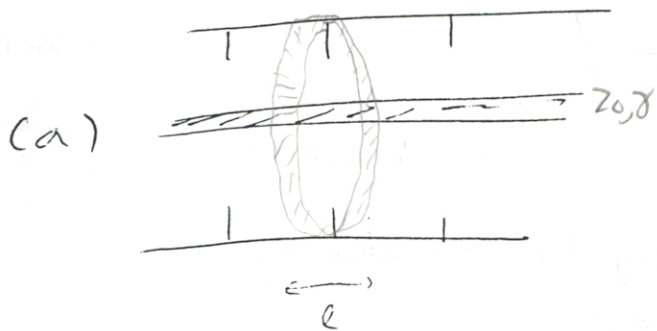[Microwave filters with periodic shunt elements]




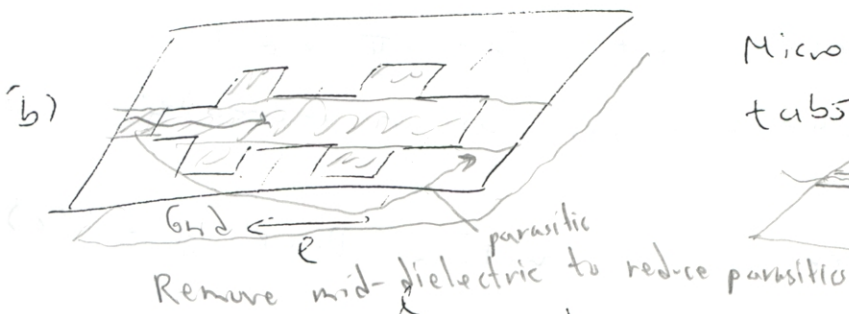Coaxial line with capacitive disks at intervals l , inductive = loop (small)



Microstrip with capacitive tabs at intervals l

Almost no parasitic coupling

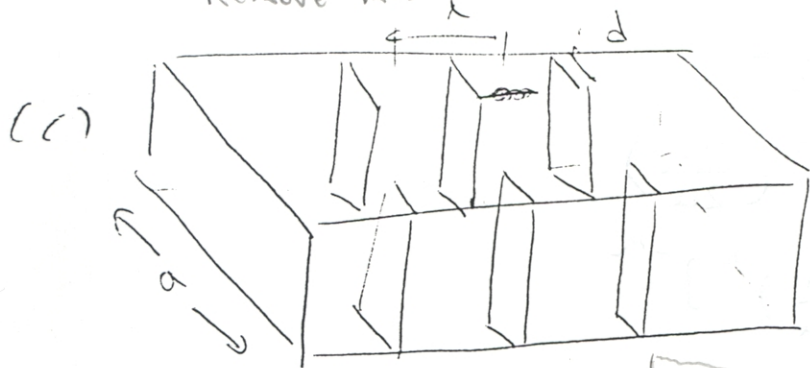


Rectangular waveguide with symmetric inductive diaphragms introduced from sides at intervals l , inductive-loop



non-symmetric inductor excites different modes - parasitics

loading capacitors are C_{disk} and assume no losses \rightarrow

$$\gamma = j\beta_{passband}$$

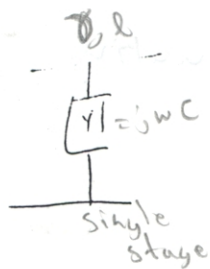

$$A_0 = D_0 = \cosh \gamma l + \left(\frac{Y}{2Y_0} \right) \sinh \gamma l$$

$$\cosh \gamma l = (A_0 + D_0) / 2 = \cosh \beta l - \frac{\omega C_d}{2Y_0} \sinh \beta l \leq 1 \text{ propagation}$$

Assume L, C the inductance and capacitance of the microstrip per unit length:

(3)

$\beta = \omega \sqrt{LC}, Z_0 = \sqrt{L/C}$

If $\beta l \ll 1$ $\xrightarrow{\text{Taylor}}$ $\cosh \Gamma \approx 1 - \frac{\omega^2 l C_0 \sqrt{LC}}{2 \sqrt{C/L}}$
 $\cos \beta l \approx 1, \sin \beta l \approx \beta l$

Passband \Leftrightarrow Imaginary $\Gamma \Leftrightarrow -1 \leq \cosh \Gamma \leq 1$

$\Rightarrow [0, \omega_c = 2 \sqrt{\frac{1}{C_0 l L}}]$

change C_0 (spacing), different materials to change size of passband

↑
cutoff angular frequency

Low Pass Filter

There are other passbands at $\beta l = n\pi, n \in \mathbb{N}$

but the passbands become narrower as n increases.

[waveguide filter with Inductive Diaphragms (c)]

Inductive diaphragms

$\frac{Y}{Y_0} = - \frac{j \lambda_g}{a} \cot^2 \left(\frac{\pi d}{2a} \right)$

$\lambda_g = \lambda \left[1 - \left(\frac{d}{2a} \right)^2 \right]^{-1/2}$

$\cosh \Gamma = \cos \left(\frac{2\pi l}{\lambda_g} \right) + \frac{\lambda_g}{2a} \cot^2 \left(\frac{\pi d}{2a} \right) \sinh \left(\frac{2\pi l}{\lambda_g} \right)$


→ High-Pass Filter (It remains attenuating even at higher frequencies)

Passband in the vicinity of $\lambda = 2a$ (Multiple passbands)

Bandpass filter in Microstrip

(4)

s.c. stubs in parallel

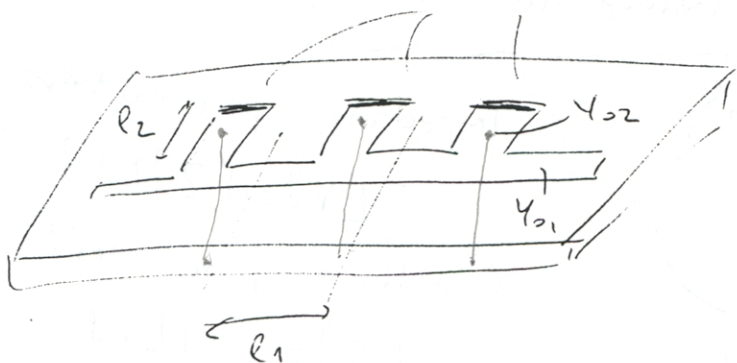

stubs can act as inductors or caps

Shunt admittance of shorted-stubs:

$$Y_{in} = -j Y_{02} \cot \beta_2 l_2$$

{

$$\cosh \Gamma = \cos \beta_1 l_1 + \frac{Y_{02}}{2Y_{01}} \cot \beta_2 l_2 \cdot \sin \beta_1 l_1$$




Bandpass filter for $\beta_2 l_2$ near $\frac{(2m+1)\pi}{2}$ where

Filtering by coupled strip lines



Optical filter

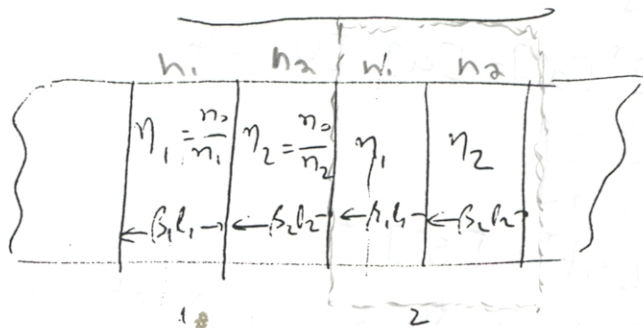


Alternating sections of transmission line of different Z_0

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \frac{\beta_1 l_1}{2} & j \eta_1 \sin \frac{\beta_1 l_1}{2} \\ j \frac{1}{\eta_1} \sin \frac{\beta_1 l_1}{2} & \cos \frac{\beta_1 l_1}{2} \end{bmatrix}$$

$$\begin{bmatrix} \cos \beta_2 l_2 & j \eta_2 \sin \beta_2 l_2 \\ j \frac{1}{\eta_2} \sin \beta_2 l_2 & \cos \beta_2 l_2 \end{bmatrix} \quad \text{--- II ---}$$

$\rightarrow A = D = \cosh \Gamma = \cos \beta_1 l_1 \cos \beta_2 l_2 - \frac{1}{2} \left(\frac{\eta_1}{\eta_2} + \frac{\eta_2}{\eta_1} \right) \sin \beta_1 l_1 \sin \beta_2 l_2$
 \rightarrow LPF

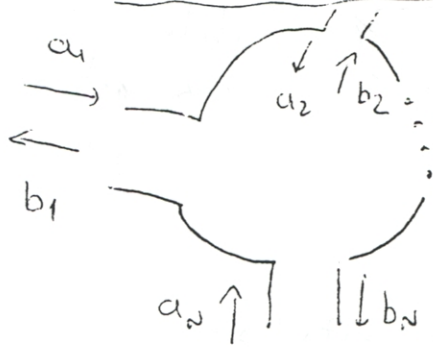N-Port Waveguide Junctions

Impedance parameters

$$[V] = [Z][I]$$

Admittance parameters

$$[I] = [Y][V]$$

(N x N Matrices)

Scattering parameters

$$[b] = [S][a]$$

N waves
leavingN waves
approachingReciprocal Networks

[Z], [Y], [S] are symmetric

$$\hookrightarrow Z_{ij} = Z_{ji}, Y_{ji} = Y_{ij}, S_{ij} = S_{ji}$$

Loss-Free Networks (lossless)

$$\text{Total Power} = \sum_{m=1}^N b_m b_m^* = \sum_{m=1}^N a_m a_m^* \Rightarrow [b]^T [b^*] = [a]^T [a^*]$$

$$\Rightarrow ([S][a])^T ([S][a])^* = [a]^T [a^*] \Leftrightarrow$$

$$\Rightarrow [a]^T [S]^T [S^*] [a]^* = [a]^T [a^*] = [a]^T [U] [a]^*$$

$$[U]: \text{unitary matrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

$$\Rightarrow [S]^T [S^*] = [U] \Rightarrow [S]^T = [S^*]^{-1}$$

(Matrices for which the transpose is the conjugate of the inverse matrix are called unitary)


$$\Rightarrow \left\{ \begin{array}{l} \sum_{n=1}^N S_{in} S_{in}^* = 1 \\ \sum_{n=1}^N S_{in} S_{jn}^* = 0, \quad i \neq j \end{array} \right. \quad \left. \begin{array}{l} \text{① } i \rightarrow \text{line (row)} \\ \text{ } j \rightarrow \text{columns} \\ \text{ } N = \# \text{ ports} \\ \text{② } \end{array} \right\} \text{Valid for reciprocal or nonreciprocal devices!!} \quad \text{②}$$

Special constraints of loss-free junctions

Equivalently:

[Z], [Y] matrices are imaginary!!
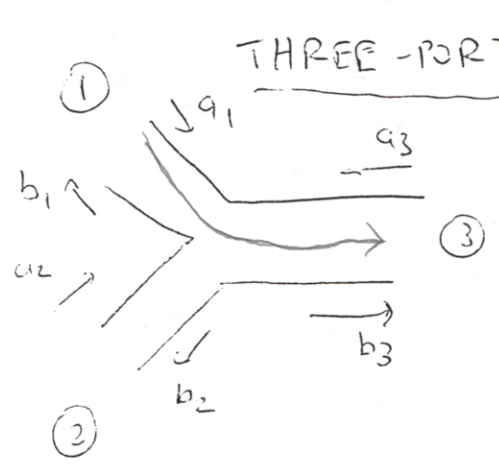
$$\begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$



Useful as a power divider or power combiner (Reciprocal)

$$S_{ij} = S_{ji}$$

$$\text{Spec. } S_{12} = 0$$

$$\begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{22} & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix} \quad \text{6 unknowns}$$

Assume sources at ①, ② with the output combined power at ③

we wish $S_{12} = 0$ (no direct interaction between two sources)

Using ① $\xrightarrow{i=1} \sum_{j=2} S_{11} S_{11}^* + S_{12} S_{12}^* + S_{13} S_{13}^* = 1 \rightarrow |S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1$


Using ② $\xrightarrow{j=2} S_{11} S_{21}^* + S_{12} S_{22}^* + S_{13} S_{23}^* = 0$

$S_{12} = 0 \rightarrow S_{13} S_{23}^* = 0$

If $S_{12} = 0 \Rightarrow S_{13} = 0$ or $S_{23} = 0$ none of the two desired couplings is eliminated. leakage from 1 \rightarrow 2

THERE IS ALWAYS INTERACTION BETWEEN TWO SOURCES

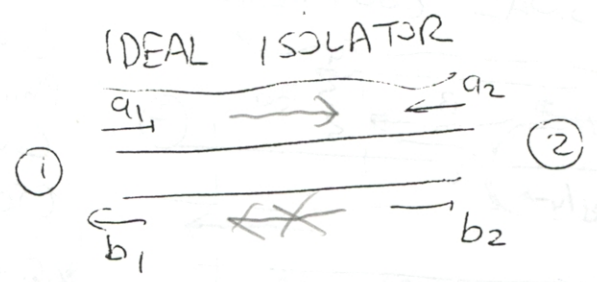(Use as a power divider ① \rightarrow ②, ③)



Should be:

(-) loss-free

(-) one-way trans. line

$$\left. \begin{aligned} S_{12} &= 0 \\ S_{21} &\neq 0 \end{aligned} \right\} \text{not reciprocal}$$

$$\textcircled{I} \xrightarrow{i=1} \left\{ \begin{aligned} S_{11} S_{11}^* + S_{12} S_{12}^* &= 1 \\ S_{11} S_{21} + S_{12} S_{22}^* &= 0 \end{aligned} \right.$$

$$\textcircled{II} \xrightarrow[\substack{i=1 \\ j=2}]{} \left\{ \begin{aligned} S_{11} S_{21} + S_{12} S_{22}^* &= 0 \\ S_{11} S_{11}^* + S_{12} S_{12}^* &= 1 \end{aligned} \right.$$


$$\textcircled{III} \text{ If } S_{12} = 0 \left\{ \begin{aligned} S_{11} &= 0 \\ \text{or } S_{21} &= 0 \end{aligned} \right.$$

$$\textcircled{IV} \text{ } \Rightarrow S_{11} \neq 0$$

$|S_{11}| = 1$

$S_{21} = 0$

IMPOSSIBLE TO BE LOSSLESS

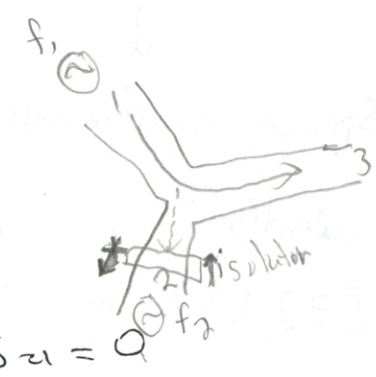

Practically: isolators use nonreciprocal elements (e.g. ferrites) but they must have dissipative elements to absorb the reflected wave

SHIFT OF REFERENCE PLANES

Shifting away from network by distance l_n per port


→ additional phase delay in S-parameters

$$S'_{ij} = S_{ij} e^{-j\beta l_i} e^{-j\beta l_j} = S_{ij} e^{-j(\beta l_i + \beta l_j)}$$

additional delay for b_i additional delay for a_j



DIRECTIONAL COUPLERS (4 ports)

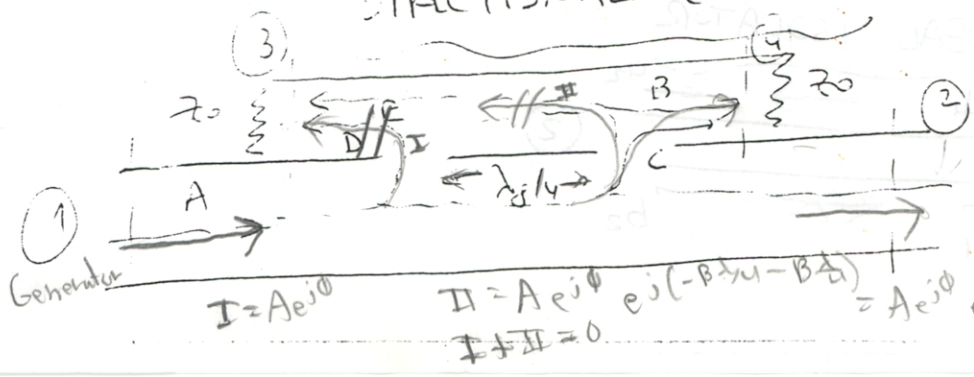

Incoming at $\textcircled{1}$
 Cancel at $\textcircled{3}$
 (Phase difference $\lambda/4 \times 2$)
 Couple at $\textcircled{2}$
 (Same length) [for equal waves]

$$I = Ae^{j\theta}$$

$$II = Ae^{j\theta} e^{j(-\beta l_1 - \beta l_2)} = Ae^{j\theta} e^{-j\pi} = -Ae^{j\theta}$$

$$I + II = 0$$

(frequency sensitive)

Similarly (2) complex + (1), (3) (4)

$$[S] = \begin{bmatrix} 0 & S_{12} & 0 & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ 0 & S_{23} & 0 & S_{34} \\ S_{14} & 0 & S_{34} & 0 \end{bmatrix}$$

4 unknowns

Assume negligible loss $\rightarrow S$ will be unitary
no reflection b/c terminate w/ Z_0

$$i=1 \rightarrow |S_{12}|^2 + |S_{14}|^2 = 1 \quad (III)$$

$$i=2 \rightarrow |S_{12}|^2 + |S_{23}|^2 = 1 \quad (IV)$$

$$i=3 \rightarrow |S_{23}|^2 + |S_{34}|^2 = 1 \quad (V)$$

$$i=4 \rightarrow |S_{14}|^2 + |S_{34}|^2 = 1 \quad (VI)$$

$$III, IV \rightarrow |S_{14}| = |S_{23}|$$

$$III, VI \rightarrow |S_{12}| = |S_{34}|$$

Choose references (2) with respect to (1) : S_{12} : positive real
(4) : S_{34} : positive real

$$S_{12} = S_{34} = a$$

Taking the zero equations (II)

$$i=1, j=3 \rightarrow S_{12} S_{23}^* + S_{14} S_{34}^* = 0 \Rightarrow S_{14} = -S_{23}^*$$

$$i=2, j=4 \rightarrow S_{12} S_{14}^* + S_{23} S_{34}^* = 0$$

Choose (4) + (1)
 $S_{14} = \text{real}$
 $S_{23} = -S_{14} = b$

$$[S] = \begin{bmatrix} 0 & a & 0 & -b \\ a & 0 & b & 0 \\ 0 & b & 0 & a \\ -b & 0 & a & 0 \end{bmatrix}$$

transmission
a: coupling factor
b: coupling factor
to the auxiliary guide




(I) $\rightarrow a^2 + b^2 = 1$

For real couplers: $S_{13}, S_{24} \neq 0$

Front-to-back ratio (Directivity) = $\frac{P_{1 \rightarrow 4}}{P_{1 \rightarrow 3}}$ Ideally = ∞

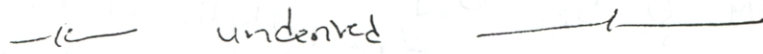Coupling to the desired terminal of auxiliary guide




→ (1) A 4-port with two pairs of noncoupling elements is completely matched.



$S_{13} = 0 = S_{24} \Rightarrow S_{11} = S_{22} = 0$

Magic-T

$a^2 = b^2 = 1/2$

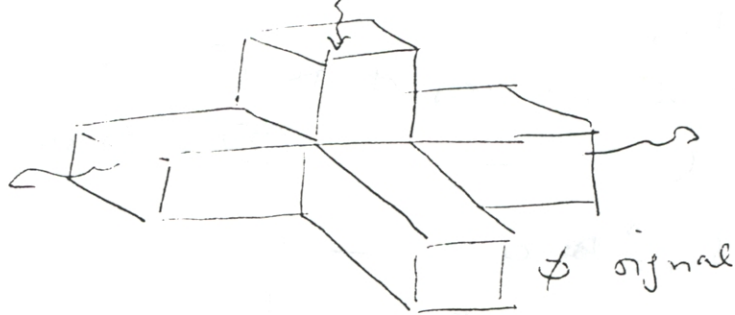

"Rat race"

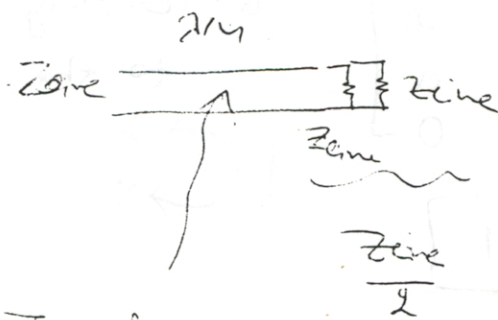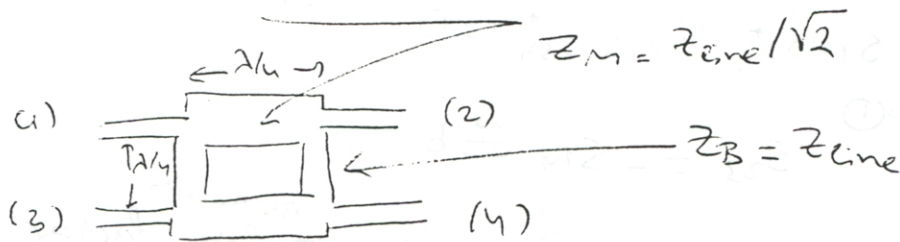

$\lambda/4$ -transformer
 $\sqrt{Z_{line} Z_{line}/2} = Z_{line}/\sqrt{2}$